

광운튜터링

RTL CODING 실습

및

FPGA에 실제 IP 설계 (UART 송수신)

2023-12-26


임성원 (광운대학교 전자재료공학과) - 조장
고종완 (광운대학교 전통신공학과) - 조원
최진혁 (광운대학교 전자재료공학과) - 조원
이민지 (광운대학교 전자재료공학과) - 조원

Contents


- Brainstorming [Sept 18 – 24]
- Specification of IP – UART [Sept 15 – Oct 30]
- Simple Chatting program [Oct 31– Nov 02]
- Capturing the Signal [Oct 31– Nov 02]
- Hardware Implementation [Oct 3 – Oct 12]
- FPGA(Quartus Synthesis and DE1-SoC board Upload) [Oct 20 – Oct 26]
- Project Integration [Oct 27 – Dec 17]
- Result and Summary [Oct 27 – Dec 17]
- Reference
- Q&A

Brainstorming [Sept 18 – 24]

 - Brainstorming to gather ideas for our project.





- Specifying IP for designing - UART

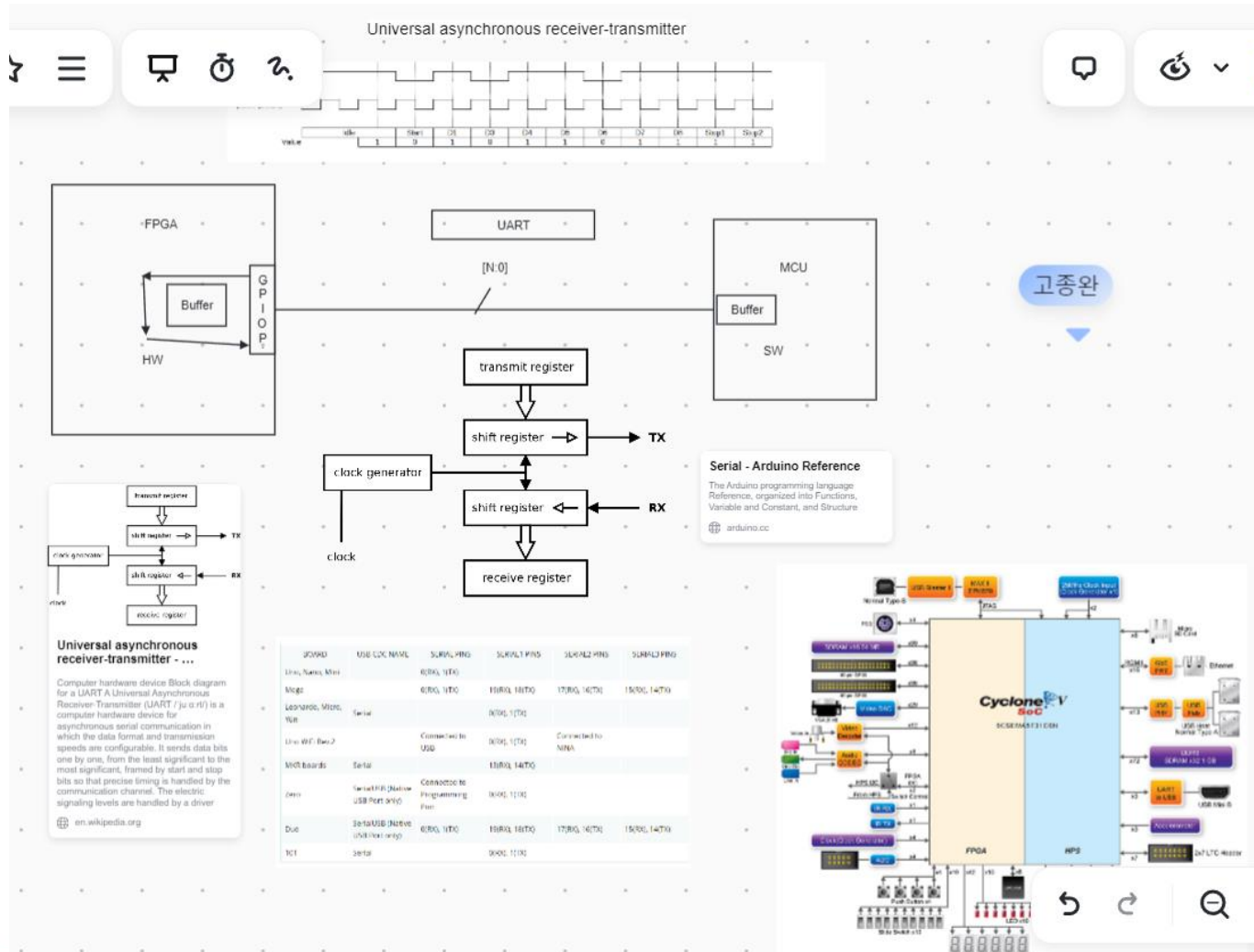

Specification of IP – UART [Oct 2– Oct 30]





- Studying basic concepts for Digital circuit designs.

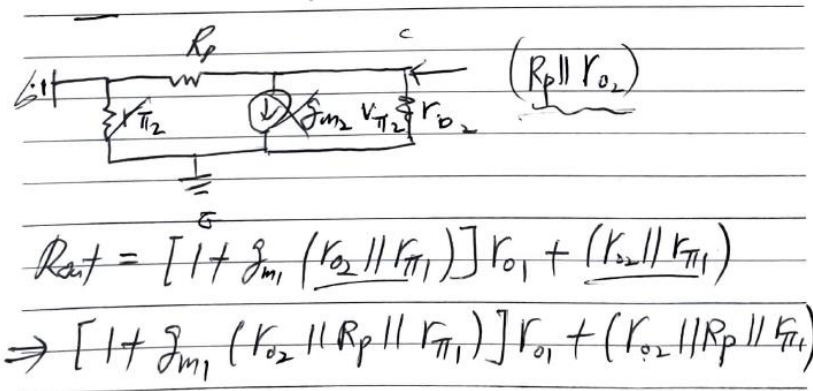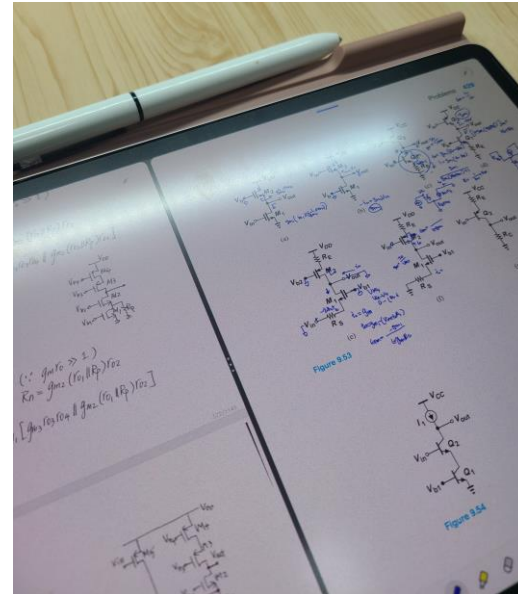[illegible][illegible]

```
for (int i = 0; i < N; i++)
{
    for (int j = 0; j < N; j++)
    {
        prove_row = i * scale_row;
        prove_row_fall = std::floor(prove_row);
        bilinear_row = prove_row - prove_row_fall;
        prove_col = j * scale_col;
        prove_col_fall = std::floor(prove_col);
        bilinear_col = prove_col - prove_col_fall;
        a = imageArray[prove_row_fall][prove_col_fall];
        b = imageArray[prove_row_fall + 1][prove_col_fall];
        c = imageArray[prove_row_fall][prove_col_fall + 1];
        d = imageArray[prove_row_fall + 1][prove_col_fall + 1];
        e = (b - a) * bilinear_row + a;
        predictor_store[i][j] = ((c - d - b - a) * bilinear_row + c - a) * bilinear_col + e;
    }
}
```


Simple Chatting program [Oct 31– Nov 02]

- Connect TX – RX and Ground pin.

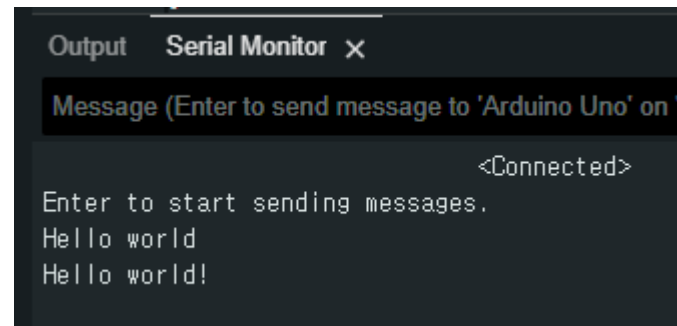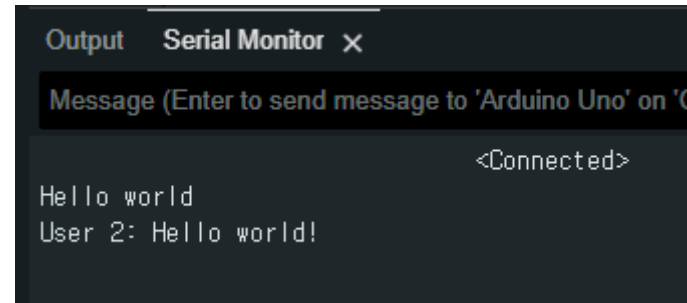  


Capturing the Signal [Oct 31– Nov 02]

- Connect Tx and Ground to Probe.

 


Hardware Implementation [Oct 3 – Oct 12]

➤ UART Block Diagram

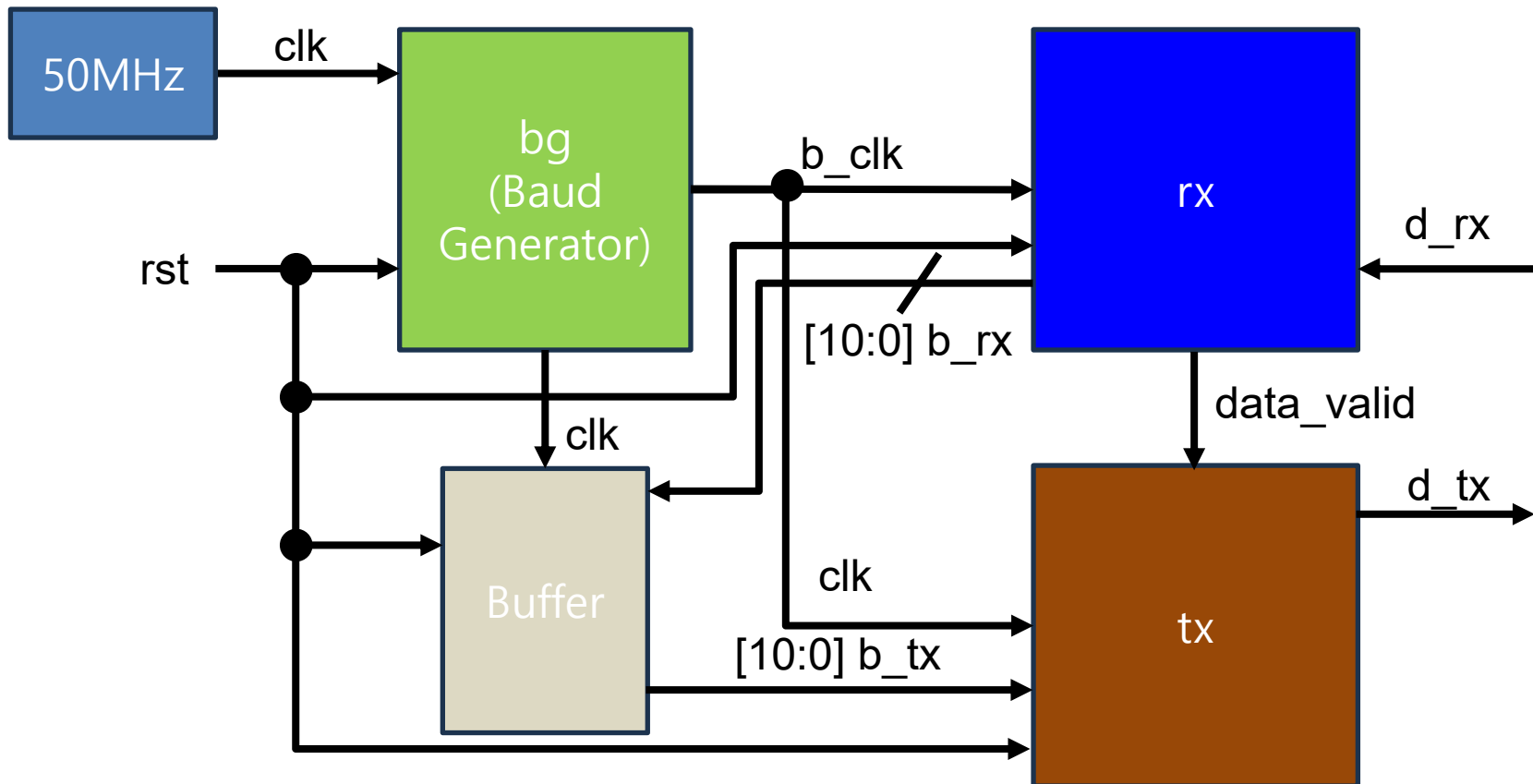


Hardware Implementation (Cont.) [Oct 3 – Oct 12]

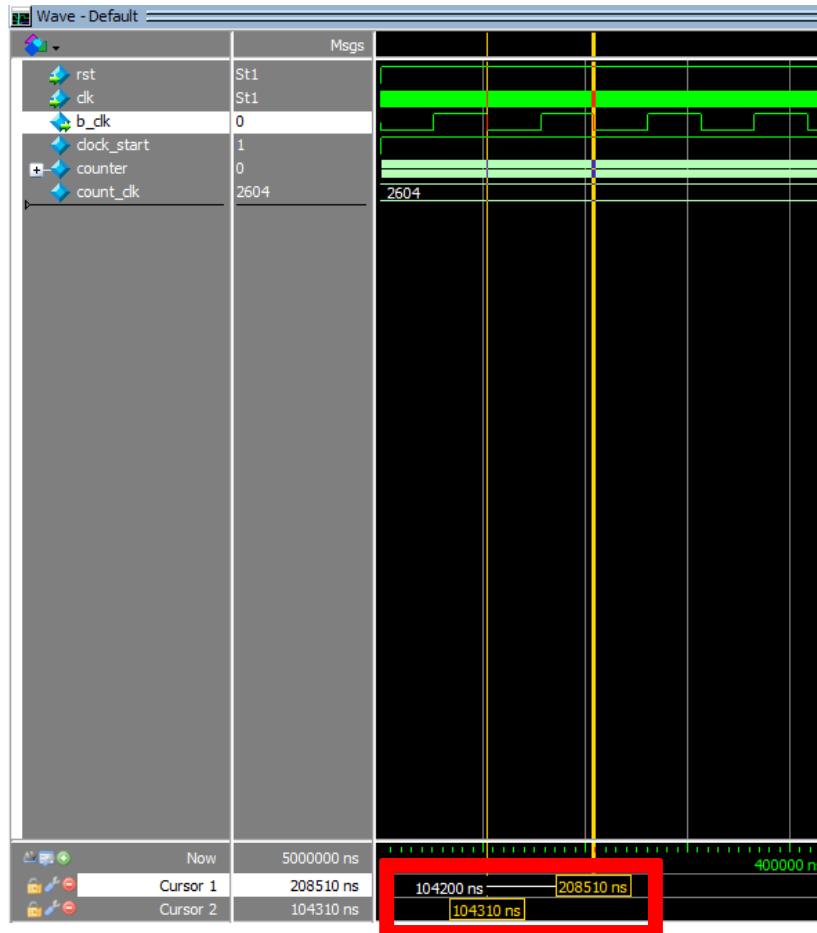- UART Baud Generator
 - 50Mhz input from FPGA Clock system => 0.02us.
 - $104.116\text{us} / 0.02\text{us} = 5208$ counts to reset clock. (104.200us)




Hardware Implementation (Cont.) [Oct 3 – Oct 12]

➤ UART Receiver State Machine

 

Hardware Implementation (Cont.) [Oct 3 – Oct 12]

➤ UART Transmitter State Machine

 


Receiver [Oct 3 – Oct 19]

- Uppercase A is being received.




Transmitter [Oct 3 – Oct 19]

- Uppercase A is being transmitted

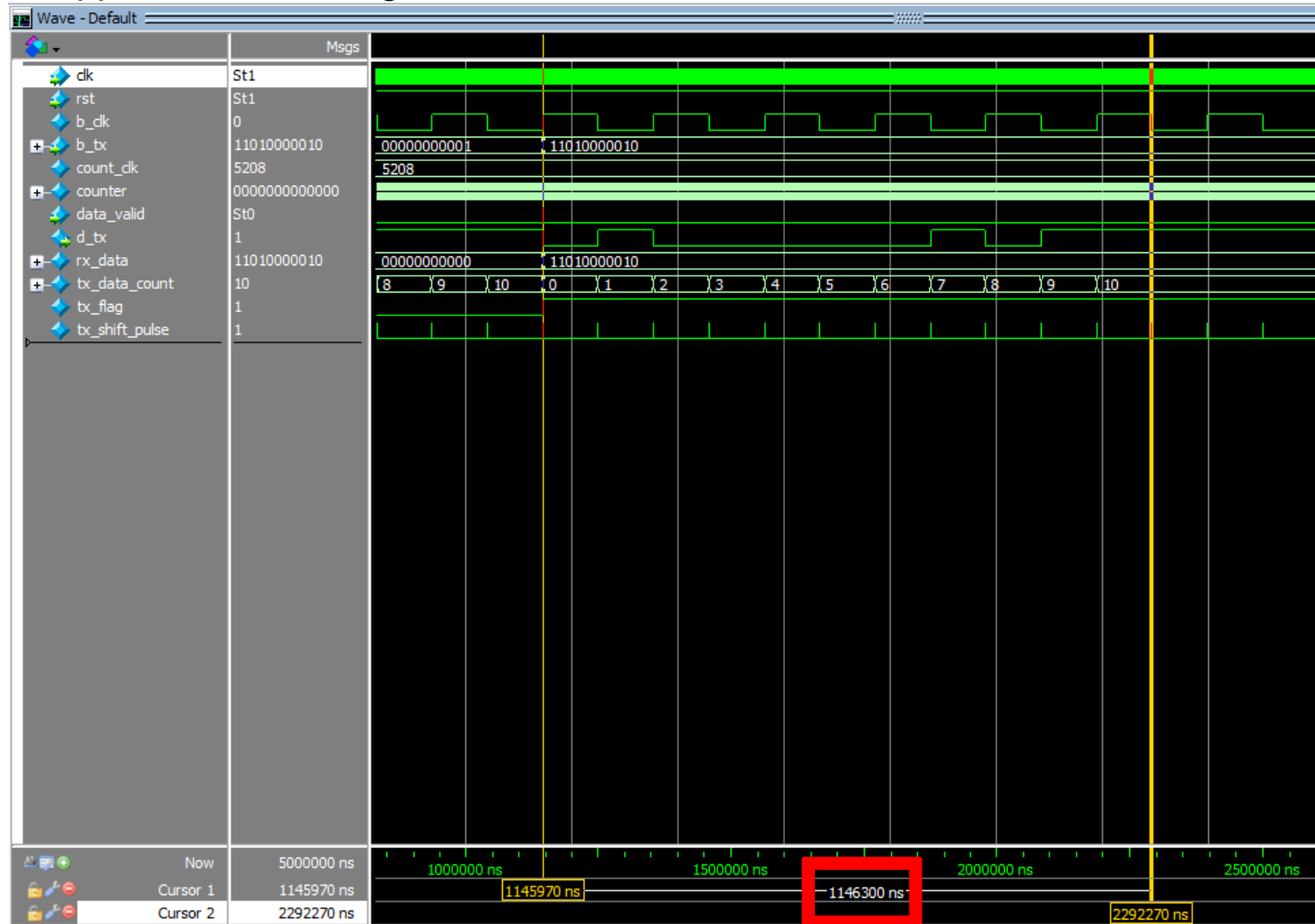

Top File [Oct 3 – Oct 19]

 - Uppercase A is being received and transmitted




FPGA [Oct 20 – Oct 26]

(Quartus Synthesis and DE1-SoC board Upload)

➤ Synthesis

	Task
✓	▼ ▶ Compile Design
✓	▼ ▶ Analysis & Synthesis
	Edit Settings
	View Report
✓	▶ Analysis & Elaboration
	> ▶ Partition Merge
	> ▶ Netlist Viewers
	> ▶ Design Assistant (Post-Mapping)
	> ▶ I/O Assignment Analysis


✓	> ▶ Fitter (Place & Route)
✓	> ▶ Assembler (Generate programming file)
✓	> ▶ TimeQuest Timing Analysis
	> ▶ EDA Netlist Writer
	Edit Settings
	▶ Program Device (Open Programmer)

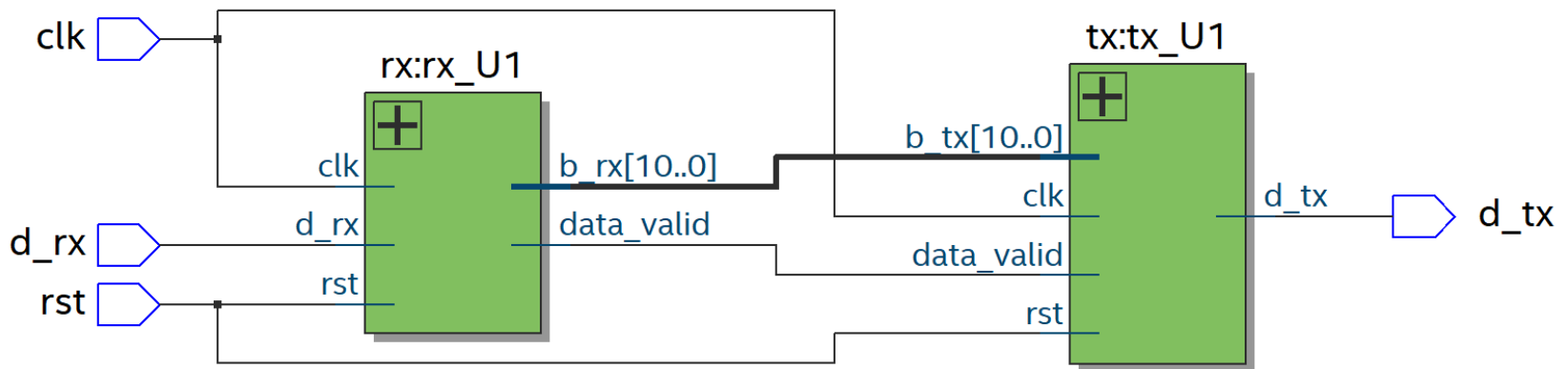

FPGA [Oct 20 – Oct 26]

(Quartus Synthesis and DE1-SoC board Upload)

➤ Pin planning.

 

Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard	Reserved	Current Strength	Slew Rate
in clk	Input	PIN_AF14	3B	B3B_N0	PIN_Y27	2.5 V (default)		12mA (default)	
in d_rx	Input	PIN_AF25	4A	B4A_N0	PIN_AB28	2.5 V (default)		12mA (default)	
out d_tx	Output	PIN_AG25	4A	B4A_N0	PIN_AA28	2.5 V (default)		12mA (default)	1 (default)
in rst	Input	PIN_AA14	3B	B3B_N0	PIN_AC29	2.5 V (default)		12mA (default)	
<<new node>>									

FPGA [Oct 20 – Oct 26]


(Quartus Synthesis and DE1-SoC board Upload)

➤ Summary

Flow Status	Successful - Sun Nov 12 20:34:08 2023
Quartus Prime Version	16.1.0 Build 196 10/24/2016 SJ Standard Edition
Revision Name	top_uart
Top-level Entity Name	top_uart
Family	Cyclone V
Device	5CSEMA5F31C6
Timing Models	Final
Logic utilization (in ALMs)	45 / 32,070 (< 1 %)
Total registers	102
Total pins	4 / 457 (< 1 %)
Total virtual pins	0
Total block memory bits	0 / 4,065,280 (0 %)
Total DSP Blocks	0 / 87 (0 %)
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 6 (0 %)
Total DLLs	0 / 4 (0 %)

Chapter 5: Level Shifter (Cont.) [Oct 27 – Dec 17]


10.2 Typical Application

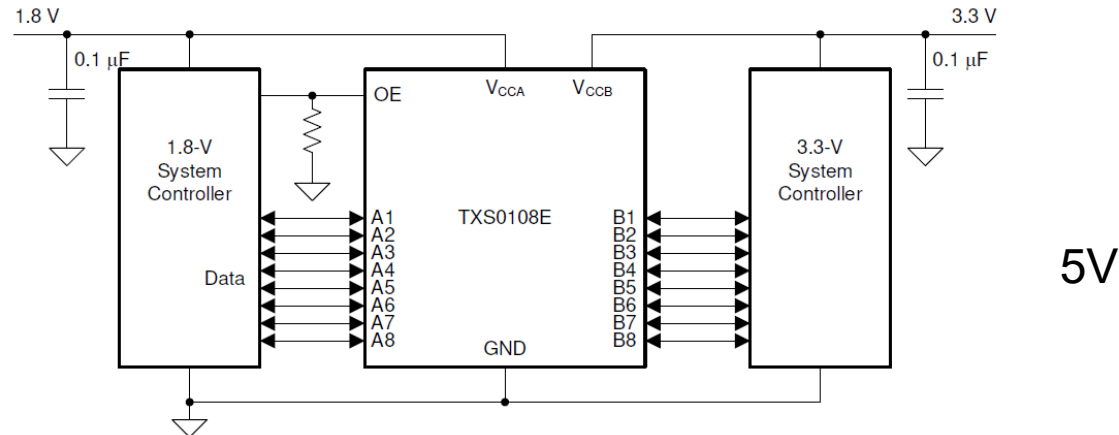

3.3V


Tx

Rx

 


5V

GND

 


Tx
Rx



Project Integration [Oct 27 – Dec 17]

 

Project Integration [Oct 27 – Dec 17]

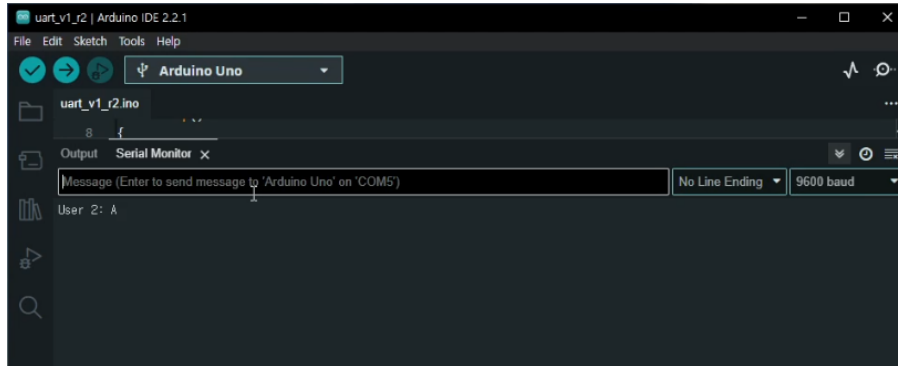

A

  

Chapter 5: Result and Summary [Oct 27 – Dec 17]

```
vlog *.v
Model Technology ModelSim - Intel FPGA Edition vlog 10.5b Compiler 2016.10 Oct 5 2016
-- Compiling module bg
-- Compiling module rx
-- Compiling module tb_rx
-- Compiling module tb_top_uart
-- Compiling module top_uart
-- Compiling module tx

Top level modules:
    tb_rx
    tb_top_uart
End time: 23:46:16 on Nov 12, 2023, Elapsed time: 0:00:00
Errors: 0, Warnings: 0
```

Not Synthesizable

Type	ID	Message
>		Running Quartus Prime Analysis & Synthesis
>		Command: quartus_map --read_settings_files=on --write_settings_files=off top
!	18236	Number of processors has not been specified which may cause overloading on :
!	20030	Parallel compilation is enabled and will use 4 of the 4 processors detected
>	12021	Found 1 design units, including 1 entities, in source file /verilog/uart/r_1
>	12021	Found 1 design units, including 1 entities, in source file /verilog/uart/r_1
>	12021	Found 1 design units, including 1 entities, in source file /verilog/uart/r_1
>	12021	Found 1 design units, including 1 entities, in source file /verilog/uart/r_1
!	10236	Verilog HDL Implicit Net warning at top_uart.v(15): created implicit net for
!	12127	Elaborating entity "top_uart" for the top level hierarchy
!	12128	Elaborating entity "rx" for hierarchy "rx:rx_u1"
!	10036	Verilog HDL or VHDL warning at rx.v(29): object "t" assigned a value but ne
!	12128	Elaborating entity "bg" for hierarchy "rx:rx_u1 bg:u_bg"
!	12128	Elaborating entity "tx" for hierarchy "tx:tx_u1"
✖	10028	Can't resolve multiple constant drivers for net "d_tx" at tx.v(136)
✖	10029	Constant driver at tx.v(122)
✖	12152	Can't elaborate user hierarchy "tx:tx_u1"
>		Quartus Prime Analysis & Synthesis was unsuccessful. 3 errors, 3 warnings
✖	293001	Quartus Prime Full Compilation was unsuccessful. 5 errors, 3 warnings

```
// data output
always @(posedge clk, negedge rst) begin
    if(!rst) begin
        d_tx <= 1'b1;
    end

    else if (tx_flag && (counter == 13'b1)) begin
        d_tx <= rx_data[tx_data_count];
    end

    else
        d_tx <= d_tx;
end


/*
always @(posedge clk, negedge rst) begin
    if(!rst) begin
        d_tx <= 1'b1;
    end

    else if (tx_flag) begin
        d_tx <= rx_data[0];
    end

    else
        d_tx <= 1'b1;
end
*/
```


Result and Summary [Oct 27 – Dec 17]

 - Future improvements
 - Loop back on one Arduino.
 - Able to transmit more than one character.
- Overview of project
 - Could understand the fundamentals of communications.
 - Understand the basic theories in action.(Nyquist Theorem, RS232...)
 - Improve the use of an oscilloscope.(How to trigger Signals.)



Reference

- UART Diagram, https://en.wikipedia.org/wiki/Universal_asynchronous_receiver-transmitter#:~:text=A%20Universal%20Asynchronous%20Receiver%2DTransmitter,and%20transmission%20speeds%20are%20configurable.
- Example of 8 – QAM, <https://www.wevolver.com/article/ baud-rates-the-most-common-baud-rates>
- ASCII code, https://web.alfredstate.edu/faculty/weimandn/miscellaneous/ascii/ascii_index.html
- Arduino Uno pinouts, <https://docs.arduino.cc/hardware/uno-rev3>
- Arduino Uno Schematics, https://www.arduino.cc/en/uploads/Main/Arduino_Uno_Rev3-schematic.pdf
- ATmega16U2 Datasheet, <https://ww1.microchip.com/downloads/en/DeviceDoc/doc7799.pdf>
- RS232 Connector, <https://www.virtual-serial-port.org/article/what-is-serial-port/rs232-pinout/>
- De1-SoC Schematic, https://people.ece.cornell.edu/land/courses/ece5760/DE1_SOC/DE1-SoC%20schematic.pdf
- De1-SoC Manual, <https://www.terasic.com.tw/cgi-bin/page/archive.pl?Language=English&CategoryNo=205&No=836&PartNo=4#contents>
- Level Shifter, <https://www.ti.com/lit/ds/symlink/txs0108e.pdf?ts=1699758033742>

Q & A
